

# Lab Report: Custom Weighted Summing & Difference Amplifier, Op-Amp Integrator, and Precision Rectifier

EE24BTECH11048-NITHIN.K  
EE24BTECH11021-ESHAN RAY

March 5, 2025

## 1 Objective

The purpose of this experiment is to design and implement a custom weighted summing and difference amplifier circuit using an operational amplifier, to study the working of an op-amp integrator, and to analyze the behavior of a precision rectifier (super diode). The circuits perform the following mathematical functions:

$$V_{out} = 2V_1 + V_2 - V_3 \quad (1)$$

$$V_{out} = 2V_1 - V_3 \quad (2)$$

$$V_{out} = -\frac{1}{RC} \int V_{in} dt \quad (3)$$

$$V_{out} = \begin{cases} 0, & V_{in} < 0 \\ V_{in}, & V_{in} > 0 \end{cases} \quad (4)$$

## 2 Components Required

- Operational amplifier (LM741, TL081, LM358, or equivalent)
- Resistors (values chosen to achieve desired functionality)
- Capacitor (for integration circuit)
- Diode (e.g., 1N4148 for precision rectifier)
- DC power supply ( $\pm 15V$ )
- Function generator (to provide input signals)
- Oscilloscope (to observe output waveforms)

## 3 Circuit Design

### 3.1 Summing and Difference Amplifier

To implement the given equations, the following resistor values are selected:

For  $V_{out} = 2V_1 + V_2 - V_3$ :

- $R_1 = R_3 = 10k\Omega$
- $R_2 = 20k\Omega$
- $R_f = 20k\Omega$

For  $V_{out} = 2V_1 - V_3$ :

- $R_1 = 10k\Omega$
- $R_3 = 10k\Omega$
- $R_f = 20k\Omega$
- No  $R_2$  needed (open circuit)

### 3.2 Op-Amp Integrator

For the integrator circuit, the component values are chosen as follows:

- $R = 10k\Omega$
- $C = 0.1\mu F$

### 3.3 Precision Rectifier

For the precision rectifier:

- Op-amp (LM358 or TL081)
- Diode (1N4148)
- Resistors (as per design)

## 4 Experimental Procedure

1. Assemble the circuits on a breadboard as per the schematic.
2. Apply  $\pm 15V$  DC power to the op-amp.
3. Use the function generator to apply the appropriate input signals.
4. Observe and record the output waveforms using an oscilloscope.
5. Compare the measured output with the theoretically expected values.

## 5 Theory and Comparison in Observations

Input Signals	Expected $V_{out}$	Measured $V_{out}$
$V_1 = 5V, V_2 = 3V, V_3 = 3V$	$2(5) + 3 - 3 = 10V$	$9.201V$
$V_1 = 5V, V_3 = 3V$	$2(5) - 3 = 7V$	$7.V$
Square wave input (Integrator)	Triangular wave output	Observed triangular wave
Small AC signal (Rectifier)	Positive half-cycle only	Observed rectified waveform

Table 1: Experimental Results

Operational amplifiers (op-amps) can be used to perform mathematical operations such as addition, subtraction, scaling, integration, and precision rectification.

### 5.1 Summing and Difference Amplifier

The inverting summing amplifier is used to achieve the desired weighted sum of input voltages. The general equation for an inverting summing amplifier is:

$$V_{out} = - \left( \frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right) \quad (5)$$

By carefully selecting resistor values, the required coefficients in the equation can be achieved. If a non-inverting input is required, a combination of inverting and summing amplifiers can be used.

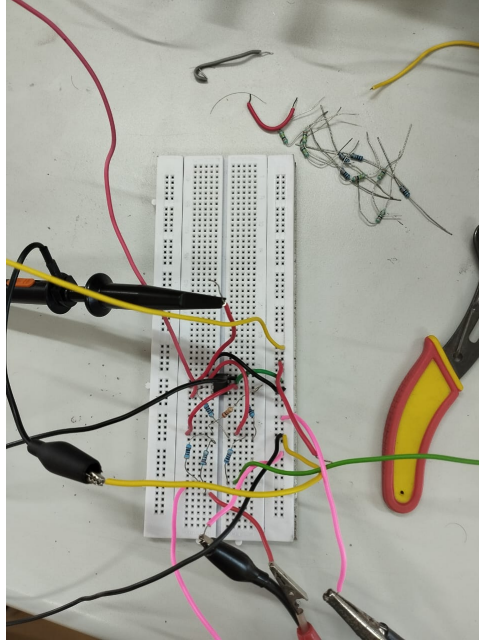


Figure 1: Circuit Diagram In Experiment

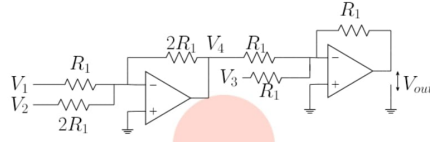


Fig. 3: Circuit Diagram

Figure 2: Circuit Diagram

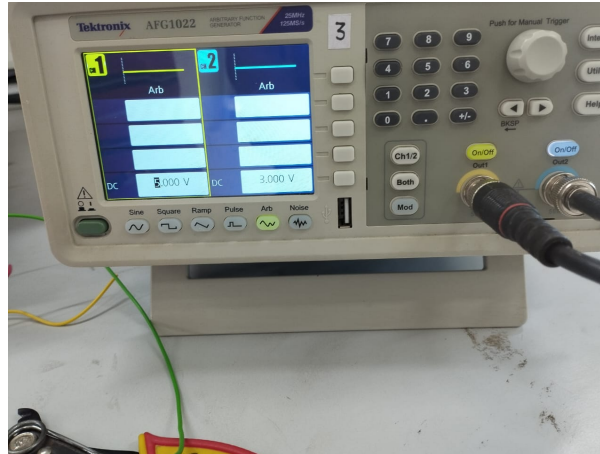


Figure 3: Voltage  $V_1 = 5V$  and  $V_2 = 3V$  for  $2V_1 + V_2 - V_3$

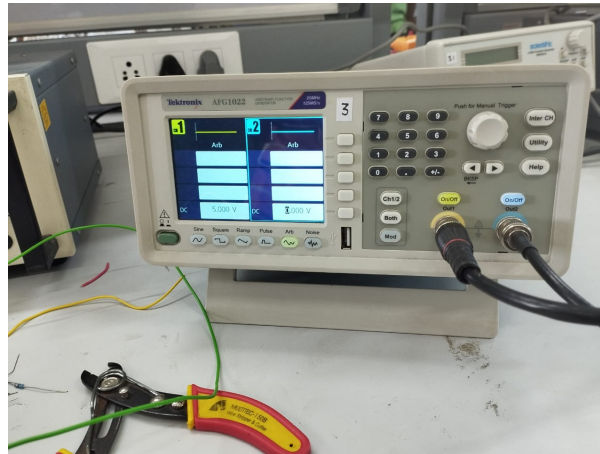


Figure 4: Voltage  $V_1 = 5V$  and  $V_2 = 0V$  for  $2V_1 - V_3$

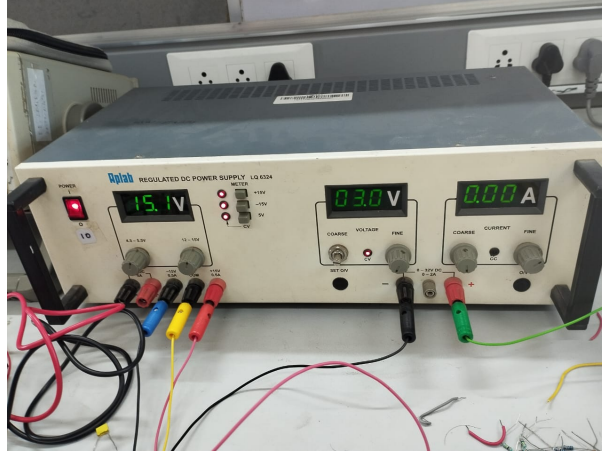


Figure 5: Voltage  $V_3 = 3V$

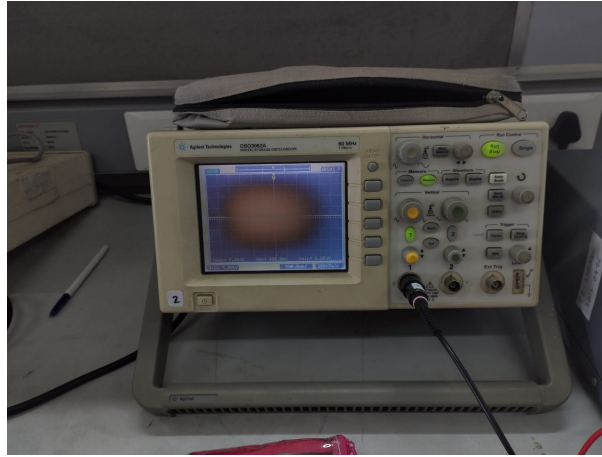


Figure 6: Observed value for  $2V_1 + V_2 - V_3$

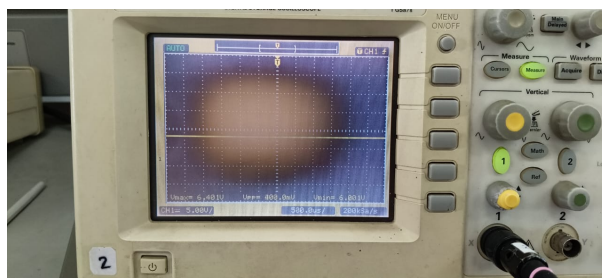


Figure 7: Observed value for  $2V_1 - V_3$

## 5.2 Op-Amp Integrator

The op-amp integrator performs the mathematical integration of an input signal. It consists of an operational amplifier with a capacitor in the feedback path instead of a resistor. The integrator follows the equation:

$$V_{out} = -\frac{1}{RC} \int V_{in} dt \quad (6)$$

This circuit converts a square wave input into a triangular wave output and is widely used in signal processing applications.

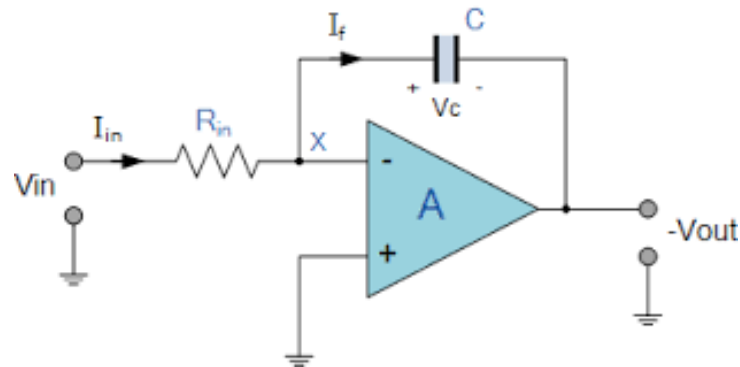


Figure 8: Circuit Diagram

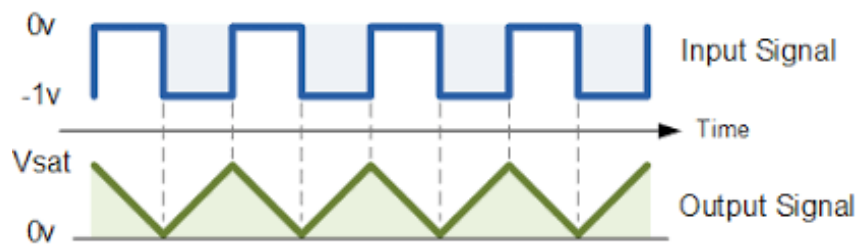


Figure 9: Input and Output Signal for Integrator



Figure 10: Input Signal In function generator

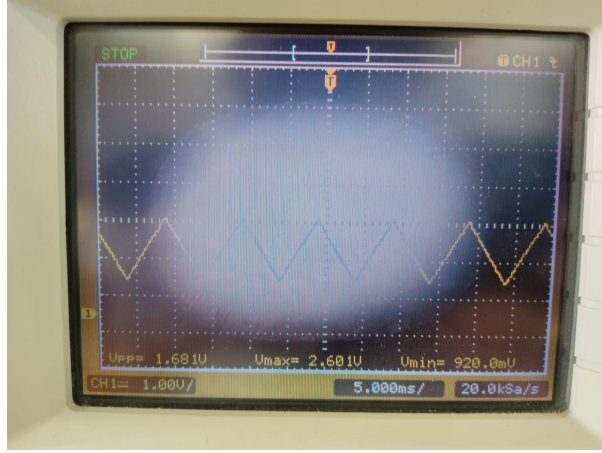


Figure 11: Observed Output Signal

The peak output voltage of an op-amp integrator with a square wave input is:

$$V_{\text{out max}} = \frac{V_{\text{in max}}}{RC} \times \frac{1}{2f}$$

Given:

$$V_{\text{in max}} = 3V, \quad R = 10k\Omega, \quad C = 0.1\mu F, \quad f = 1kHz$$

Substituting the values:

$$\begin{aligned} V_{\text{out max}} &= \frac{3}{(10k\Omega \times 0.1\mu F)} \times \frac{1}{2 \times 1000} \\ &= \frac{3}{(10^4 \times 10^{-7})} \times \frac{1}{2000} \\ &= \frac{3}{10^{-3}} \times \frac{1}{2000} \\ &= 3000 \times \frac{1}{2000} \\ &= 1.5V \end{aligned}$$

Thus, the peak output voltage is:

$$V_{\text{out max}} = 1.5V$$

The observed peak output is  $2.6V - 0.92V = 1.68V$ .

### 5.3 Precision Rectifier (Super Diode)

A precision rectifier, or super diode, eliminates the voltage drop problem of conventional diodes, enabling rectification of small AC signals. The circuit consists of an op-amp controlling a diode. For a half-wave rectifier:

$$V_{\text{out}} = \begin{cases} 0, & V_{\text{in}} < 0 \\ V_{\text{in}}, & V_{\text{in}} > 0 \end{cases} \quad (7)$$



A full-wave rectifier can be implemented using an additional summing stage to combine the positive and inverted negative portions.

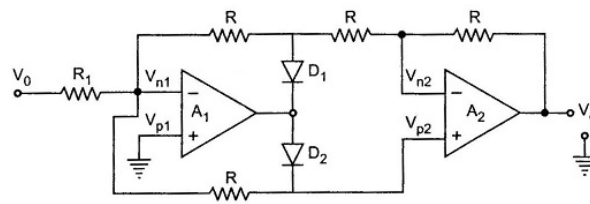


Fig. 2.63 Full wave rectifier

Figure 12: Circuit Diagram for halfwave

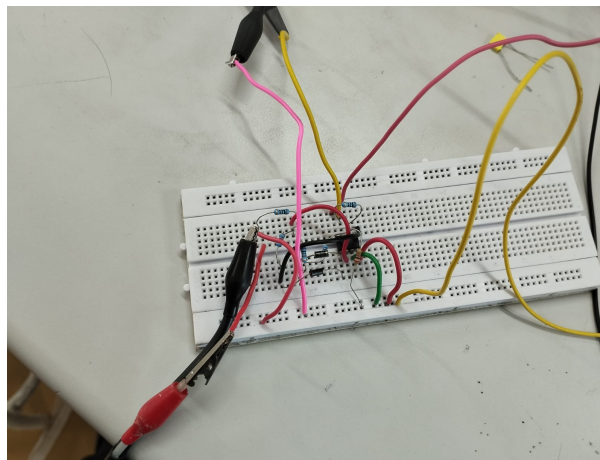


Figure 13: Circuit Diagram In Experiment for fullwave

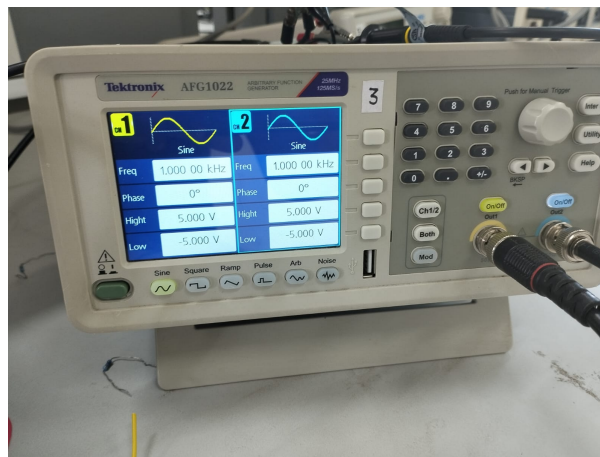


Figure 14: Input Values given by function generator for fullwave



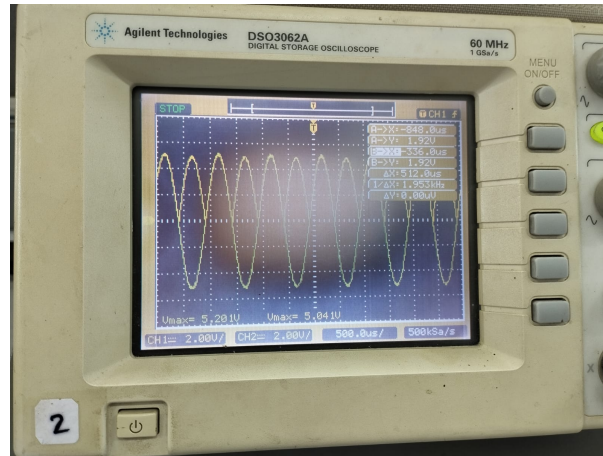


Figure 15: Observed Fullwave Rectification

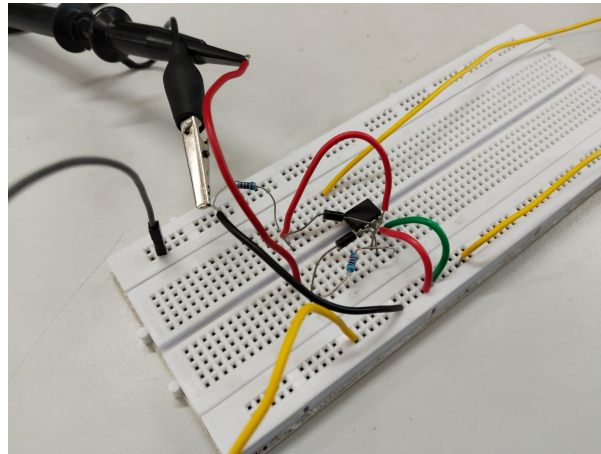


Figure 16: Circuit Diagram In Experiment for halfwave

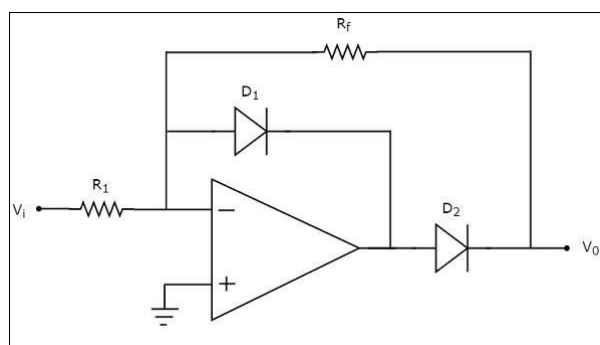


Figure 17: Circuit Diagram for halfwave



Figure 18: Input for Halfwave Rectifier

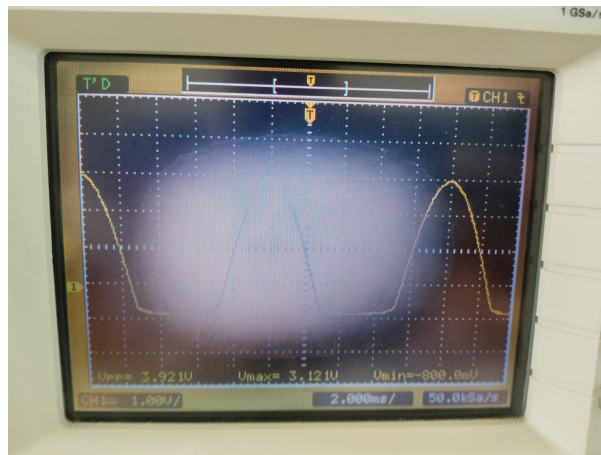


Figure 19: Observed Halfwave Precision Rectification

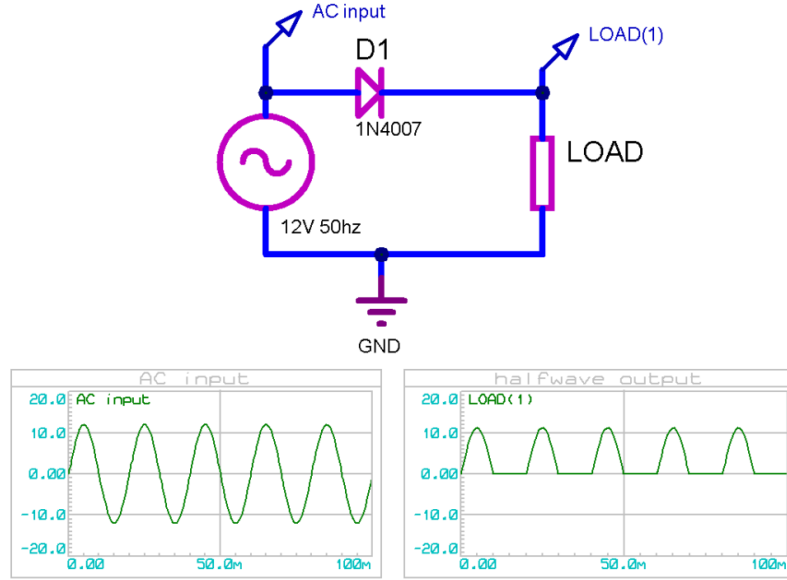


Figure 20: Circuit Diagram for Halfwave Rectification using diode and resistor(values in this are not the one's used for experiment)



Figure 21: Observed Halfwave Rectification without opamp

There is the 0.7V threshold voltage of diode hence for given input of 1.2V we should get  $1.2V - 0.7V = 0.4V$ . The observed value is 0.344V. There is Leakage of current in the diode that's why there is less voltage than theoretical value.

## 6 Conclusion

The experimental results confirm the correct operation of the summing amplifier, op-amp integrator, and precision rectifier. The precision rectifier successfully eliminates the voltage drop of conventional diodes, enabling accurate rectification of small AC signals.